

### 電子學(一) HW3

1. Consider a CMOS process for which  $L_{min} = 0.18 \mu\text{m}$ ,  $t_{ox} = 4 \text{ nm}$ ,  $\mu_n = 450 \text{ cm}^2/\text{V} \cdot \text{s}$ . and  $V_{tn} = 0.5 \text{ V}$ .
  - (a) Find  $C_{ox}$  and  $k'_n$ .
  - (b) For an NMOS transistor with  $W/L = 2.4 \mu\text{m}/0.18 \mu\text{m}$ , calculate the values of  $V_{OV}$ ,  $V_{GS}$  and  $V_{DSmin}$  needed to operate the transistor in the saturation region with a current  $I_D = 0.1 \text{ mA}$ .
  - (c) For the device in (b), find the values of  $V_{OV}$  and  $V_{GS}$  required to cause the device to operate as a  $500\text{-}\Omega$  resistor for very small  $V_{DS}$ .
  
2. A particular MOSFET for which  $V_{tn} = 0.4 \text{ V}$  and  $k'_n(W/L) = 2\text{mA}/\text{V}^2$  is to be operated in the saturation region. If  $I_D$  is to be  $50 \mu\text{A}$ , find the required  $V_{GS}$  and the minimum required  $V_{DS}$ . Repeat for  $I_D = 200 \mu\text{A}$ .
  
3. The table above lists the terminal voltages of a PMOS transistor in six cases, labeled a, b, c, d, e and f. The transistor has  $V_{tp} = -1 \text{ V}$ . Complete the table entries.

	$V_S$	$V_G$	$V_D$	$V_{SG}$	$ V_{OV} $	$V_{SD}$	Region of operation
a	+2	+2	0	1			
b	+2	+1	0				
c	+2	0	0				
d	+2	0	+1				
e	+2	0	+1.5				
f	+2	0	+2				

4. For the circuit in Fig.E5.10, assume that  $Q_1$  and  $Q_2$  are matched except for having different widths,  $W_1$  and  $W_2$ . Let  $V_t = 0.5V$ ,  $k'_n = 0.4mA/V^2$ ,  $L_1 = L_2 = 0.36\mu m$ ,  $W_1 = 1.8\mu m$ , and  $\lambda = 0$ .

(a) Find the value of  $R$  required to establish a current of  $100\mu A$  in  $Q_1$ .

(b) Find  $W_2$ , and  $R_2$ , so that  $Q_2$  operates at the edge of saturation with a current of  $0.5\text{ mA}$ .

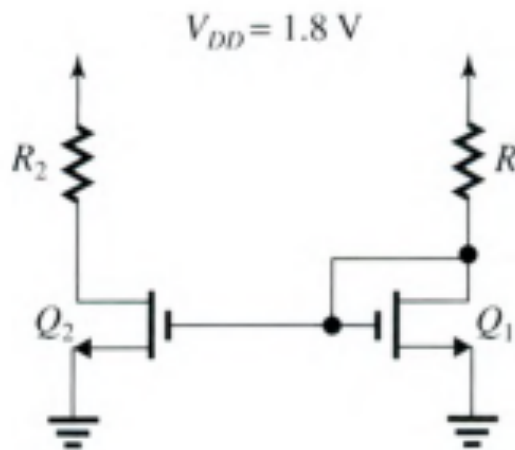


Figure E5.10