


HW5

1)

Proof that π -model is equivalent to T-model (MOSFET). (Neglect channel length modulation)

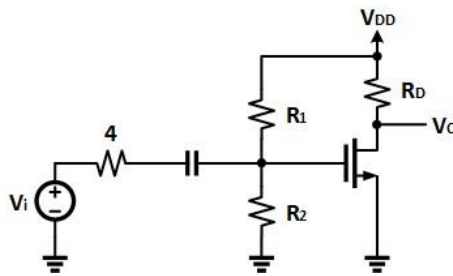2)

For the circuit as shown, the parameters are: $V_{DD} = 10V$, $R_1 = 70.9k\Omega$, $R_2 = 29.1k\Omega$, and $R_D = 5k\Omega$. The transistor parameters are: $V_{tn} = 1.5V$, $k_n = 0.5mA/V^2$, and $\lambda = 0.01V^{-1}$. Determine the small-signal voltage gain, input resistance, and output resistance of the common-source amplifier.



3)

A CS amplifier utilizes a MOSFET with $\mu_n C_{ox} = 400 \mu A/V^2$ and $W/L=10$. It is biased at $I_D = 320 \mu A$ and uses $R_D = 10k\Omega$. Find R_{in} , A_V , and R_o . Also, if a load resistance of $10k\Omega$ is connected to the output, what overall voltage gain A_V is realized? Now, if a 0.2-V peak sine-wave signal is required at the output, what must the peak amplitude of v_{sig} be?

4)

A common-source amplifier utilizes a MOSFET operated at $V_{OV} = 0.25 V$. The amplifier feeds a load resistance $R_L = 15k\Omega$. The designer selects $R_D = 2R_L$. If it is required to realize an overall voltage gain A_V of $-10 V/V$ what g_m is needed? Also specify the bias current I_D . If, to increase the output signal swing, R_D is reduced to $R_D = R_L$, what does A_V become?